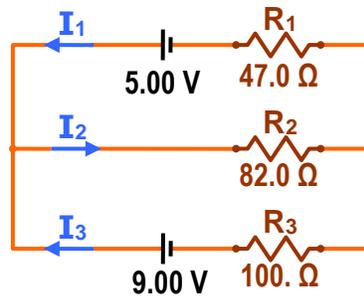


## Kirchhoff's Rules

Consider the following circuit:



A. Using Kirchhoff's Rules, write the equation for:

- 1) the top loop
- 2) the bottom loop
- 3) the current

B. Evaluate the following:

- |          |             |
|----------|-------------|
| 1) $I_1$ | 4) $V_{R1}$ |
| 2) $I_2$ | 5) $V_{R2}$ |
| 3) $I_3$ | 6) $V_{R3}$ |

---

### SOLUTIONS

A. (1)  $-R_1 I_1 + 5 - R_2 I_2 = 0$  (2)  $-R_2 I_2 - R_3 I_3 + 9 = 0$  (3)  $I_1 + I_3 = I_2$

B. (1) 10.3 mA (2) 55.1 mA (3) 44.8 mA (4) 0.483 V (5) 4.52 V (6) 4.48 V

